






**Habib University**  
**Electrical Engineering Department**  
**Dhanani School of Science & Engineering**


Course	EE - 211 - Basic Electronics
Semester	Fall 2022
Section	Section 1
Exam	Quiz - 2a
Instructor	Dr. Ahmad Usman
Total Marks	10

**Question - 1 (CLO 2, Points: 5+5)**

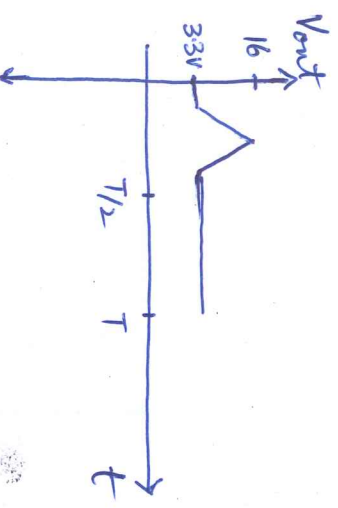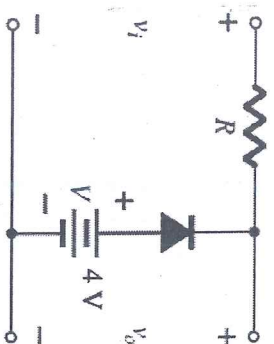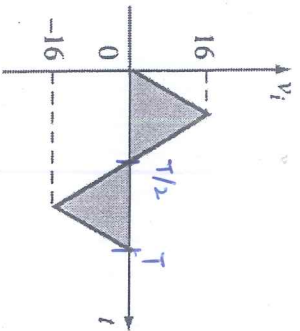- a) Determine  $V_O$  for the following circuit shown below. Draw the waveform for the circuit. Clearly label your waveform. Assume  $V_{D,ON} = 0.7V$ .



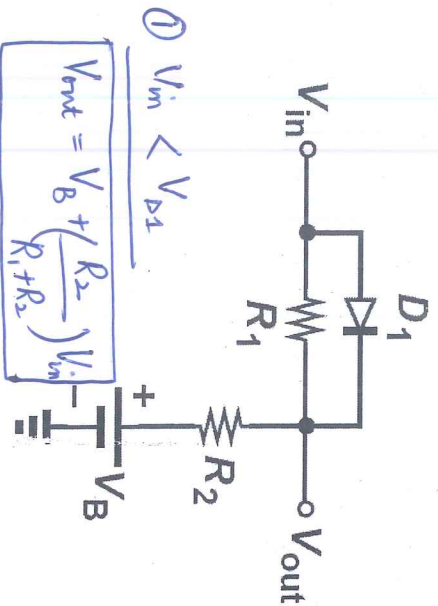- b) Draw the input-output characteristics of the circuit shown in the figure below. Use the constant-voltage model for the diode i.e.,  $V_{D,ON} = 0.7V$  and assume  $V_B = 2V$ .




①  $V_{in} < V_{D1}$

$$V_{out} = V_B + \left( \frac{R_2}{R_1 + R_2} \right) V_{in}$$

②  $V_{in} > V_{D1}$

$$V_{out} \neq V_{in} + V_B$$

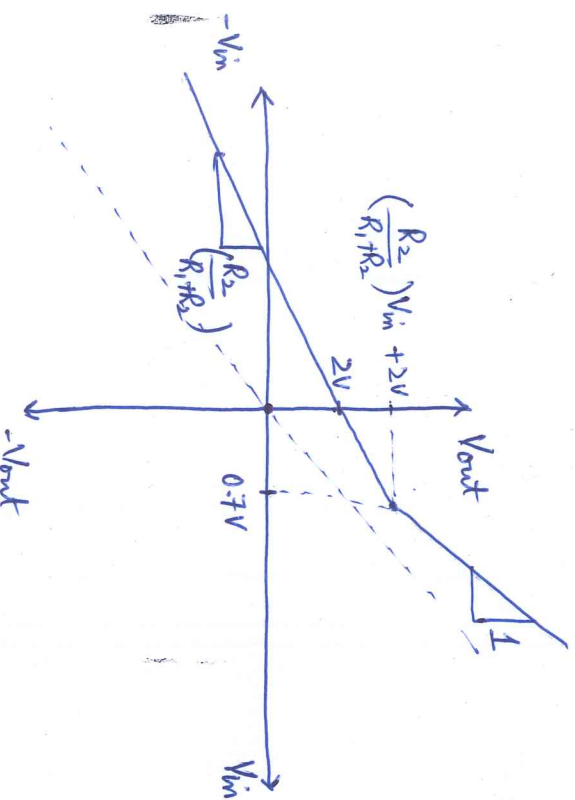



# Habib University




## Electrical Engineering Department

### Dhanani School of Science & Engineering


Course	EE - 211 - Basic Electronics
Semester	Fall 2022
Section	Section 1
Exam	Quiz - 2b
Instructor	Dr. Ahmad Usman
Total Marks	10

#### Question - 1 (CLO 2, Points: 5+5)

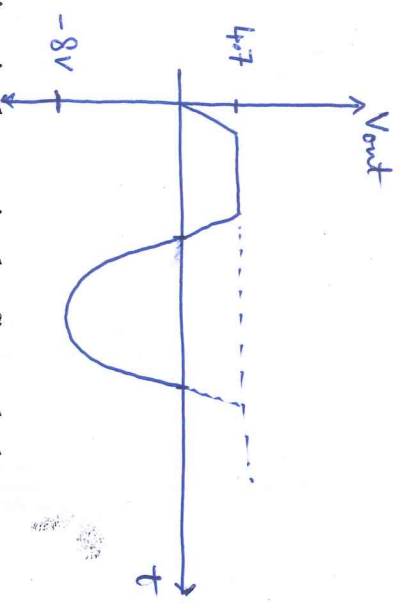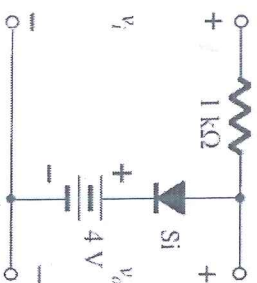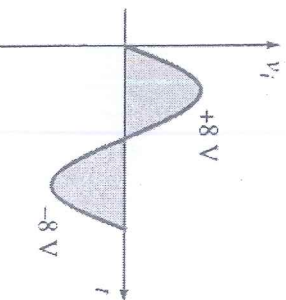a) Determine  $V_O$  for the following circuit shown below. Draw the waveform for the circuit. Clearly label your waveform. Assume  $V_{D,ON} = 0.7V$ .



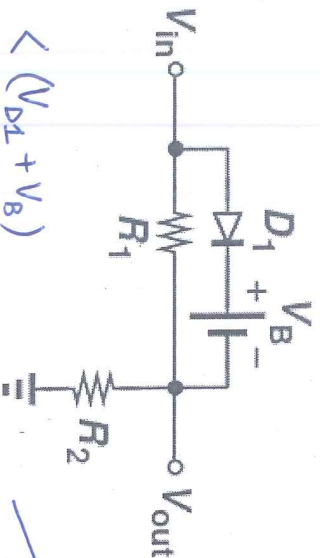
b) Draw the input-output characteristics of the circuit shown in the figure below. Use the constant-voltage model for the diode i.e.,  $V_{D,ON} = 0.7V$  and assume  $V_B = 2V$ .



①  $V_{in} < (V_{D1} + V_B)$

$$\boxed{V_{out} = \left( \frac{R_2}{R_1 + R_2} \right) V_{in}}$$
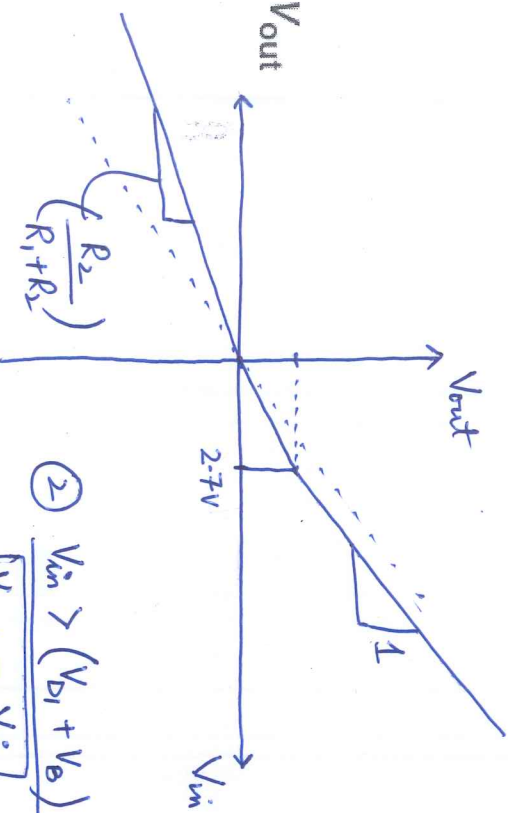
$$\frac{V_{out}}{V_{in}} = \left( \frac{R_2}{R_1 + R_2} \right) < 1$$



②  $V_{in} > (V_{D1} + V_B)$

$$\boxed{V_{out} = V_{in}}$$

$$\frac{V_{out}}{V_{in}} = 1$$