



Habib University

Electrical Engineering Department

Dhanani School of Science & Engineering

| | |
|-------------|------------------------------|
| Course | EE – 211 – Basic Electronics |
| Semester | Fall 2022 |
| Section | Section L2 |
| Exam | Midterm Exam – 1 |
| Instructor | Dr. Ahmad Usman |
| Total Marks | 25 |

Name: Solution Student ID: _____

Question # 1 (CLO – 1 – Points: 5, 2.5 + 2.5)

A pn junction is operating in forward bias.

- (a) To obtain a current of 1 mA with an applied voltage of 750mV, what should I_s be and how should it be chosen?

$$I_D = I_s \left(\exp \frac{V_D}{V_T} - 1 \right)$$

$$1\text{m} = I_s \left(\exp \frac{750\text{m}}{26\text{m}} - 1 \right)$$

$$I_s = 2.9667 \times 10^{-16} \text{ A}$$

$$I_s = A q n_i^2 \left[\frac{D_n}{N_A L_n} + \frac{D_p}{N_D L_p} \right]$$

$$I_s \propto A$$

The I_s can be chosen by controlling the cross-sectional area of the diode.

- (b) If the diode cross section area is doubled, what voltage yields a current of 1mA?

$$I_s \propto A$$

$$2A \propto 2I_s$$

$$I_s = 2 (2.9667 \times 10^{-16})$$

$$I_D = 1\text{mA}$$


$$\rightarrow 1\text{m} = 2 (2.9667 \times 10^{-16}) \left[\exp \frac{V_D}{26\text{m}} - 1 \right]$$

$$V_D = 0.7319 \text{ V}$$

$$V_D = 731.9 \text{ mV}$$

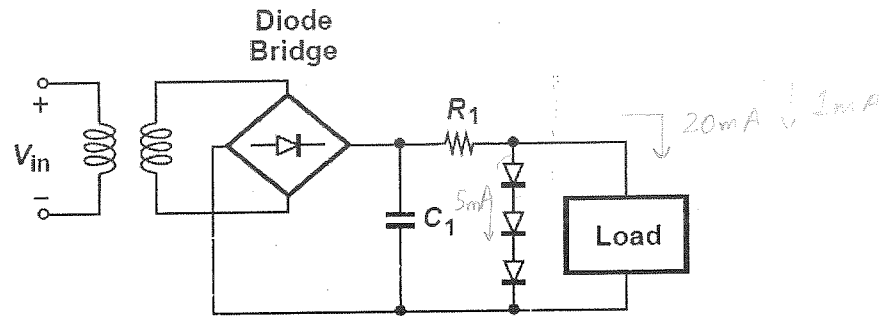Question # 2 (CLO – 1 – Points: 5)

In the figure shown below, the diodes are carrying a 5mA current and the load draws 20 mA of current. If the load current increases by 1 mA, what is the change in the total voltage across the three diodes? Assume that the three diodes are similar diodes, having resistance of r_d . Assume R_1 to be greater than $3r_d$. Remember $r_d = V_T / I_D$.



$$r_d = \frac{V_T}{I_D} = \frac{26\text{m}}{5\text{m}} = 5.2\Omega$$

$$\text{Total } r_d = 3r_d = \boxed{15.6\Omega}$$

$$\frac{\Delta I_D}{\Delta V_D} = \frac{I_D}{V_T}$$

$$\Delta V_D = \left(\frac{26\text{m}}{5\text{m}} \right) (1\text{mA}) \times 3$$


$$\boxed{\Delta V_D = 15.6\text{mV}}$$

Question # 3 (CLO – 2 – Points: 7.5, 5 + 2.5)

An oscillator application requires a variable capacitance with the characteristic shown in the figure.

Assume the area of the device as $1000 \mu\text{m}^2$.

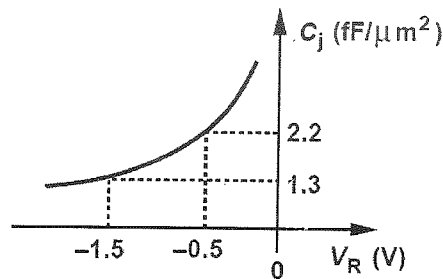Hint: You have to assume a value of N_A (say $2 \times 10^{18} \text{ cm}^{-3}$) after calculating the ratio of $(N_A N_D / N_A + N_D)$.



(a) Determine N_A and N_D .

$$2.2 \text{ fF}/\mu\text{m}^2 = \frac{C_{j0}}{\sqrt{1 + \frac{0.5}{V_0}}} \quad \text{--- (1)}$$

$$1.3 \text{ fF}/\mu\text{m}^2 = \frac{C_{j0}}{\sqrt{1 + \frac{1.5}{V_0}}} \quad \text{--- (2)}$$

From Eq (1), we get

$$4.84 \left(\frac{\text{fF}}{\mu\text{m}^2} \right)^2 = \frac{C_{j0}^2}{1 + \frac{0.5}{V_0}}$$

$$4.84 + \frac{2.42}{V_0} = C_{j0}^2 \quad \text{--- (3)}$$

$$1.69 + \frac{2.535}{V_0} = C_{j0}^2 \quad \text{--- (4)}$$

$$4.84 + \frac{2.42}{V_0} = 1.69 + \frac{2.535}{V_0}$$

$$(4.84 - 1.69) = \frac{2.535}{V_0} - \frac{2.42}{V_0}$$

$$V_0 = (0.115) / 3.15$$

$$V_0 = 0.0365 \text{ V}$$

$$C_{j0}^2 = 4.84 + \frac{2.42}{0.0365} \left(\frac{\text{fF}}{\mu\text{m}^2} \right)^2$$

$$C_{j0} = 8.4336 \frac{\text{fF}}{\mu\text{m}^2}$$

$$C_{j0} = 8.4336 \text{ fF} \times 1000$$

$$C_{j0} = 8.4336 \text{ pF} @ V_R = 0$$

(b) Calculate the value of inductance required to oscillate this device a 5 GHz (at $V_R = 0\text{V}$).

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\pi [5 \times 10^9] = \frac{1}{\sqrt{L \times C_{j0}}}$$

$$L = 120.1398 \text{ pH}$$

$$C_{j0} = \sqrt{\frac{\epsilon_{si} q}{2} \left(\frac{N_A N_D}{N_A + N_D} \right) \left(\frac{1}{V_0} \right)}$$

$$\frac{N_A N_D}{N_A + N_D} = 3.1343 \times 10^{17} \text{ cm}^{-3}$$


$$\text{Let } N_A = 2 \times 10^{18} \text{ cm}^{-3}$$

$$\text{then } N_D = 3.071 \times 10^{17} \text{ cm}^{-3}$$

Question # 4 (CLO – 3 - Points: 7.5, 2 + 1.5 + 4)


Design a dc power supply using a bridge-rectifier to develop a certain dc voltage across the load R_L . The current through the load is 500 mA. Use a stepdown transformer whose primary side is connected to 240 V (RMS) at a mains frequency of 50 Hz.

(a) Draw the circuit diagram.

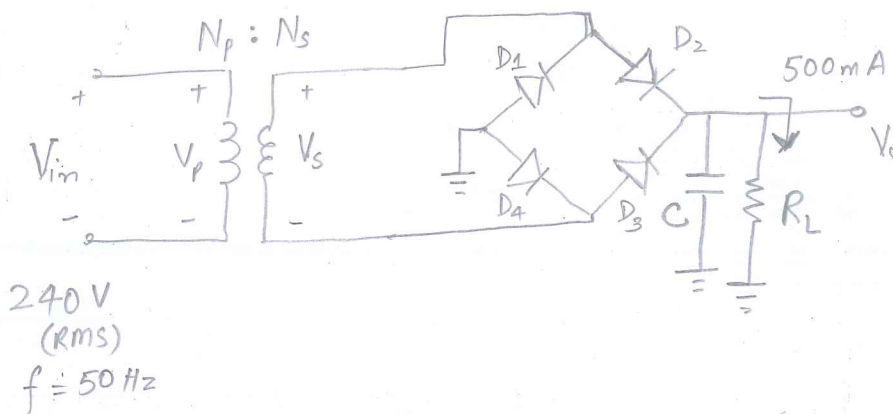

$$V_o^{(dc)} = \frac{2 V_o(\max)}{\pi}$$

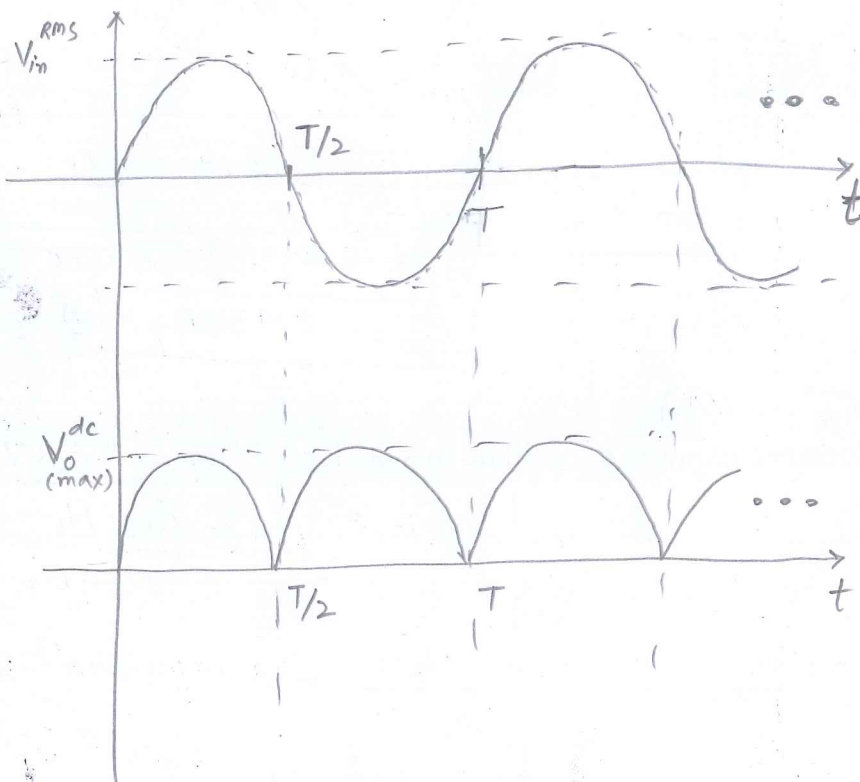(b) Draw the input and output voltage waveforms of the designed dc power supply.



(c) Specify the PIV-rating, $I_{d,max}$ rating, and the power-rating of the diodes. Assume practical silicon diodes ($V_{D,ON} = 0.7V$), safety factor of 1.5, and $R_L = 15 \Omega$. Show all your working properly.

Note: You don't need to derive the formulas. Just use them for your calculations.

$$V_{dc} = I_L R_L = (500 \text{ m})(15) = 7.5 \text{ V}$$

$$V_{o(max)} = \frac{\pi V_{dc}}{2} = \frac{7.5 \times 3.142}{2} = \boxed{11.7825 \text{ V}}$$

$$V_s = V_{o(max)} + V_{\text{drop diode}}$$

OR

$$V_s = V_{o(max)} + 2V_{\text{drop diode}}$$

$$V_s = 11.7825 + 0.7$$

$$\boxed{V_s = 12.4825 \text{ V}}$$

← RMS →

$$\boxed{V_s = 13.1825 \text{ V}}$$

$$V_s^{\text{Peak}} = \sqrt{2} V_s^{\text{RMS}}$$

$$\boxed{V_s^{\text{Peak}} = 17.6529 \text{ V}}$$

$$V_s^{\text{Peak}} = \sqrt{2} V_s^{\text{RMS}}$$

$$\boxed{V_s^{\text{Peak}} = 18.6428 \text{ V}}$$

PIV Rating:

$$V_{o(max)} = 11.7825 \times 1.5$$

$$\boxed{V_{o(max)}^{\text{PIV}} \geq 17.673 \text{ V}}$$

$I_{d(max)}$ Rating:

$$I_{o(max)}^{\text{dc}} = \frac{\pi I_{dc}}{2} = 785.5 \text{ mA}$$

$$\boxed{I_{o(max)}^{\text{dc}} \geq 1.17825 \text{ A}}$$

$P_{d(max)}$ Rating:

$$P_{d(max)}^{\text{dc}} = I_{d(max)}^{\text{dc}} V_{\text{diode}} = 785.5 \times 0.7$$

$$P_{d(max)}^{\text{dc}} = 549.85 \text{ mW}$$

$$\boxed{P_{d(max)}^{\text{dc}} \geq 824.775 \text{ mW}}$$